



Eta Kappa Nu
Beta Nu Chapter



RPI HKN ECSE Honor Society

ECSE 1010 M1K Mentoring


Topic: Discharging Parallel Capacitors





Circuit Setup

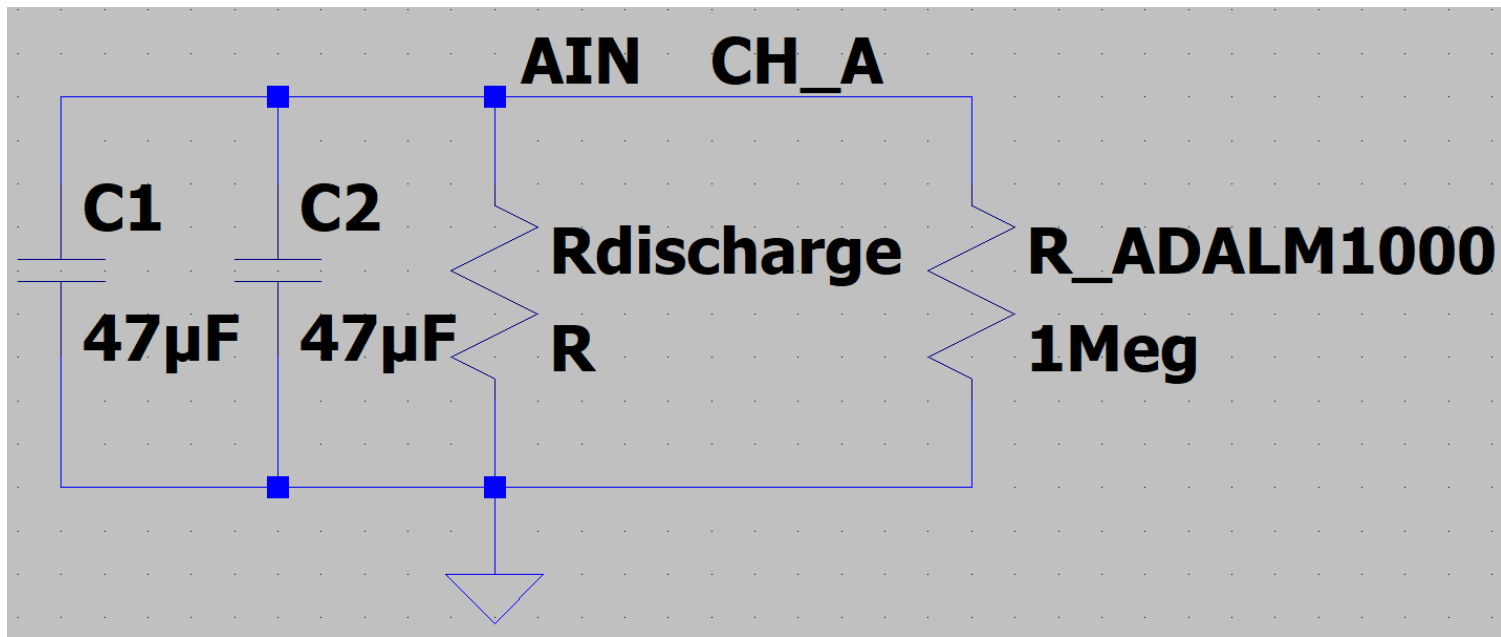Time Constant $\tau = RC = 10\text{ms}, 1\text{s}, 10\text{s}; R = ?$






Experimental Setup

AIN and CH A
wires
(Red & White)

Connection
wires
(Green)

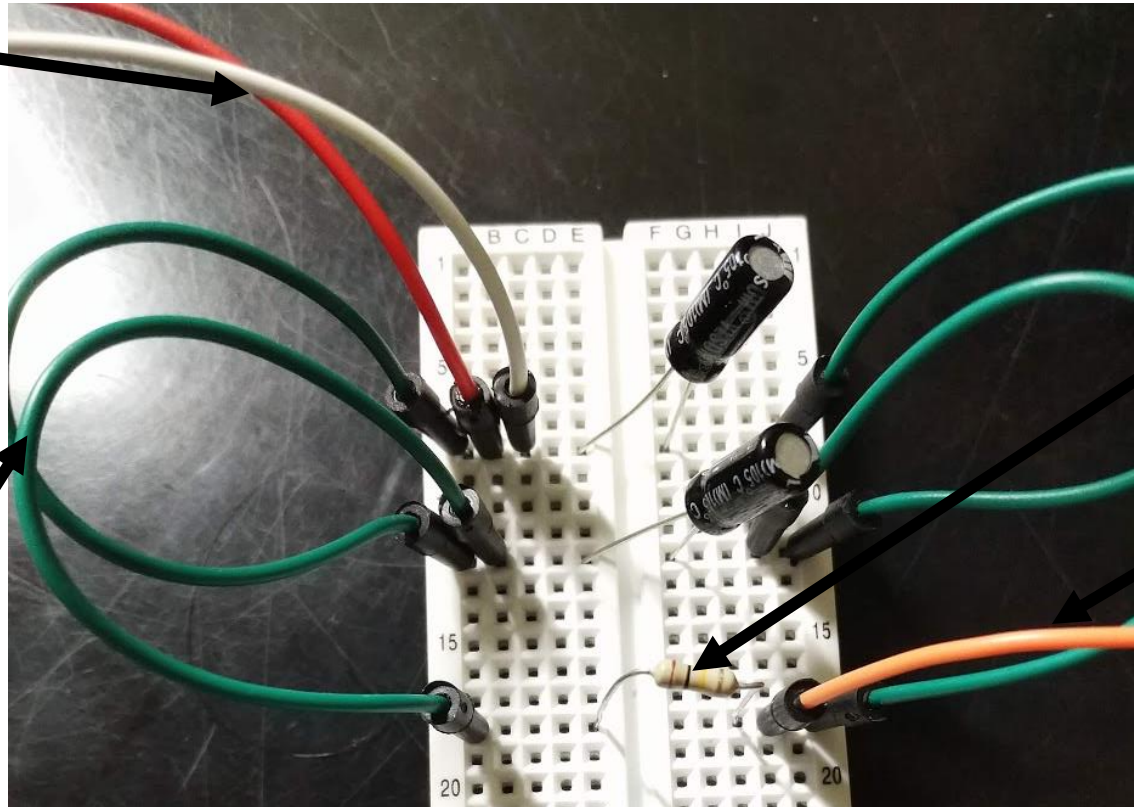

Rdischarge
eg: 100Ω

GND
(Orange)



Data Collection

- **Open Alice Data Logger tool**
- **Set a 5V CH A source**
- **Select “Log to file” option (for later)**
- **After a few seconds, turn CH A off**
- **Should see capacitor discharge**
- **What happens at τ , 5τ ?**



MATLAB Analysis

- Open the collected data
- File can be found:
C/ALM_Software/M1K/StripChart.csv
- Trim your data points
- Import the csv into MATLAB
- Plot your data!
- Try comparing with calculated voltage values: $V(t) = V_0 e^{-t/\tau}$



MATLAB Analysis

